

# SIMPLIFICATION OF BOOLEAN EXPRESSIONS

**Dr. Suneth Pathirana**

B.Sc.(UWU-CST)(Hons), M.Sc.(AI)(Moratuwa), MIEEE, Ph.D.(MSU)

Senior Lecturer

Department of Computer Science & Informatics

Uva Wellassa University of Sri Lanka

[suneth@uwu.ac.lk](mailto:suneth@uwu.ac.lk)

# Basic Rules for Boolean Algebra

## Basic Rules of Boolean Algebra


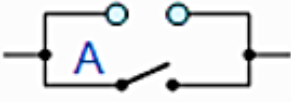
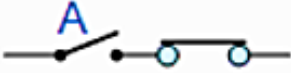
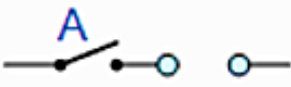
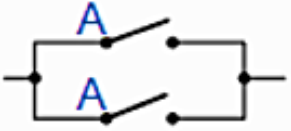
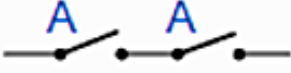
1. $A + 0 = A$	7. $A \cdot A = A$
2. $A + 1 = 1$	8. $A \cdot \overline{A} = 0$
3. $A \cdot 0 = 0$	9. $\overline{\overline{A}} = A$
4. $A \cdot 1 = A$	10. $A + AB = A$
5. $A + A = A$	11. $A + \overline{A}B = A + B$
6. $A + \overline{A} = 1$	12. $(A + B)(A + C) = A + BC$

## DeMorgan's Theorem





$$\overline{(AB)} = (\overline{A} + \overline{B})$$

$$\overline{(A + B)} = (\overline{A} \cdot \overline{B})$$

# Explained: in Detail

Boolean Expression	Description	Equivalent Switching Circuit	Boolean Algebra Law or Rule
$A + 1 = 1$	A in parallel with closed = "CLOSED"		Annulment
$A + 0 = A$	A in parallel with open = "A"		Identity
$A \cdot 1 = A$	A in series with closed = "A"		Identity
$A \cdot 0 = 0$	A in series with open = "OPEN"		Annulment
$A + A = A$	A in parallel with A = "A"		Idempotent
$A \cdot A = A$	A in series with A = "A"		Idempotent

# Explained: in Detail

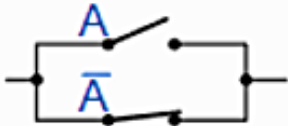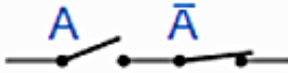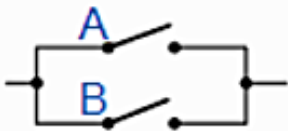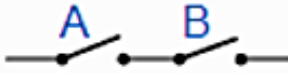$\text{NOT } \bar{A} = A$	NOT NOT A (double negative) = "A"		Double Negation
$A + \bar{A} = 1$	A in parallel with NOT A = "CLOSED"		Complement
$A \cdot \bar{A} = 0$	A in series with NOT A = "OPEN"		Complement
$A+B = B+A$	A in parallel with B = B in parallel with A		Commutative
$A \cdot B = B \cdot A$	A in series with B = B in series with A		Commutative
$\overline{A+B} = \bar{A} \cdot \bar{B}$	invert and replace OR with AND		de Morgan's Theorem
$\overline{A \cdot B} = \bar{A} + \bar{B}$	invert and replace AND with OR		de Morgan's Theorem

# Comprehensive Version Ahead!

1.	Law of Identity	$A = A$ $\overline{A} = \overline{A}$
2.	Commutative Law	$A \cdot B = B \cdot A$ $A + B = B + A$
3.	Associative Law	$A \cdot (B \cdot C) = A \cdot B \cdot C$ $A + (B + C) = A + B + C$
4.	Idempotent Law	$A \cdot A = A$ $A + A = A$
5.	Double Negative Law	$\overline{\overline{A}} = A$
6.	Complementary Law	$A \cdot \overline{A} = 0$ $A + \overline{A} = 1$
7.	Law of Intersection	$A \cdot 1 = A$ $A \cdot 0 = 0$
8.	Law of Union	$A + 1 = 1$ $A + 0 = A$
9.	DeMorgan's Theorem	$\overline{AB} = \overline{A} + \overline{B}$ $\overline{A + B} = \overline{A} \cdot \overline{B}$
10.	Distributive Law	$A \cdot (B + C) = (A \cdot B) + (A \cdot C)$ $A + (BC) = (A + B) \cdot (A + C)$
11.	Law of Absorption	$A \cdot (A + B) = A$ $A + (AB) = A$
12.	Law of Common Identities	$A \cdot (\overline{A} + B) = AB$ $A + (\overline{A}B) = A + B$

# Simplifications

- Ⓢ Using the above laws, simplify the following expression:
- Ⓢ  $(A + B)(A + C)$

# Simplifications

$$Q = (A + B).(A + C)$$

$$A.A + A.C + A.B + B.C \quad - \text{Distributive law}$$

$$A + A.C + A.B + B.C \quad - \text{Idempotent AND law (A.A = A)}$$

$$A(1 + C) + A.B + B.C \quad - \text{Distributive law}$$

$$A.1 + A.B + B.C \quad - \text{Identity OR law (1 + C = 1)}$$

$$A(1 + B) + B.C \quad - \text{Distributive law}$$

$$A.1 + B.C \quad - \text{Identity OR law (1 + B = 1)}$$

$$Q = A + (B.C) \quad - \text{Identity AND law (A.1 = A)}$$



# Simplifications


⊗ Simplify the following:

$$\oplus C + \overline{BC}$$

$$\oplus \overline{AB}(\overline{A} + B)(\overline{B} + B)$$

$$\oplus (A + C)(AD + A\overline{D}) + AC + C$$

$$\oplus \overline{A}(A + B) + (B + AA)(A + \overline{B})$$

  $C + \overline{BC}$

$$\oplus \overline{A}B(\overline{A} + B)(\overline{B} + B)$$

$$\oplus (A + C)(AD + A\overline{D}) + AC + C$$

$$\oplus \overline{A}(A + B) + (B + AA)(A + \overline{B})$$

# Answers

Simplify:  $C + \overline{BC}$ :

Expression

$C + \overline{BC}$

$C + (\overline{B} + \overline{C})$

$(C + \overline{C}) + \overline{B}$

$T + \overline{B}$

$T$

Rule(s) Used

Original Expression

DeMorgan's Law.

Commutative, Associative Laws.

Complement Law.

Identity Law.

# Answers

Simplify:  $\overline{A}B(\overline{A} + B)(\overline{B} + B)$ :

Expression

$$\overline{A}B(\overline{A} + B)(\overline{B} + B)$$

$$\overline{A}B(\overline{A} + B)$$

$$(\overline{A} + \overline{B})(\overline{A} + B)$$

$$\overline{A} + \overline{B}B$$

$$\overline{A}$$

Rule(s) Used

Original Expression

Complement law, Identity law.

DeMorgan's Law

Distributive law. This step uses the fact that or distributes over and. It can look a bit strange since addition does not distribute over multiplication.

Complement, Identity.

# Answers

Simplify:  $(A + C)(AD + A\bar{D}) + AC + C$ :

Expression

$$(A + C)(AD + A\bar{D}) + AC + C$$

$$(A + C)A(D + \bar{D}) + AC + C$$

$$(A + C)A + AC + C$$

$$A((A + C) + C) + C$$

$$A(A + C) + C$$

$$AA + AC + C$$

$$A + (A + C)C$$

$$A + C$$

Rule(s) Used

Original Expression

Distributive.

Complement, Identity.

Commutative,  
Distributive.

Associative,  
Idempotent.

Distributive.

Idempotent, Identity,  
Distributive.

Identity, twice.



# Answers

Simplify:  $\overline{A}(A + B) + (B + AA)(A + \overline{B})$ :

Expression

$$\overline{A}(A + B) + (B + AA)(A + \overline{B})$$

$$\overline{A}A + \overline{A}B + (B + A)A + (B + A)\overline{B}$$

$$\overline{A}B + (B + A)A + (B + A)\overline{B}$$

$$\overline{A}B + BA + AA + B\overline{B} + A\overline{B}$$

$$\overline{A}B + BA + A + A\overline{B}$$

$$\overline{A}B + AB + AT + A\overline{B}$$

$$\overline{A}B + A(B + T + \overline{B})$$

$$\overline{A}B + A$$

$$A + \overline{A}B$$

$$(A + \overline{A})(A + B)$$

$$A + B$$

Rule(s) Used

Original Expression

Idempotent ( $AA$  to  $A$ ), then Distributive, used twice.

Complement, then Identity. (Strictly speaking, we also used the Commutative Law for each of these applications.)

Distributive, two places.

Idempotent (for the  $A$ 's), then Complement and Identity to remove  $B\overline{B}$ .

Commutative, Identity; setting up for the next step.

Distributive.

Identity, twice (depending how you count it).

Commutative.

Distributive.

Complement, Identity.

# Karnaugh Maps

# Karnaugh maps

- ② The Karnaugh map provides a simple and straight-forward method of minimising boolean expressions
- ② With the Karnaugh map Boolean expressions having up to four and even six variables can be simplified

# Karnaugh maps

- Ⓢ A Karnaugh map provides a pictorial method of grouping together expressions with common factors and therefore eliminating unwanted variables
- Ⓢ The Karnaugh map can also be described as a special arrangement of a truth table

# Karnaugh maps

- ② The correspondence between the Karnaugh map and the truth table for the general case of a two variable problem

A	B	F
0	0	a
0	1	b
1	0	c
1	1	d

Truth Table.

		A	
		0	1
B	0	a	b
	1	c	d

F.

# Karnaugh maps

## © Example

A	B	F
0	0	0
0	1	1
1	0	1
1	1	1

Truth Table.

		A	
B	0	1	
0	0	1	←
1	1	1	

F.

# Using Karnaugh maps for simplifications

@ Example:

➤  $Z = A\bar{B} + AB$

@ Using algebraic simplification,

➤  $Z = A(\bar{B} + B)$

➤  $Z = A$

@ Consider the following map:

@ Referring to the map above, the two adjacent 1's are grouped together

		A	
		0	1
B	0		1
	1		1

# Using Karnaugh maps for simplifications


		A	
		0	1
B	0		1
	1		1

- Ⓢ Through inspection it can be seen that variable B has its true and false form within the group
- Ⓢ This eliminates variable B leaving only variable A which only has its true form
- Ⓢ The minimised answer therefore is  $Z = A$


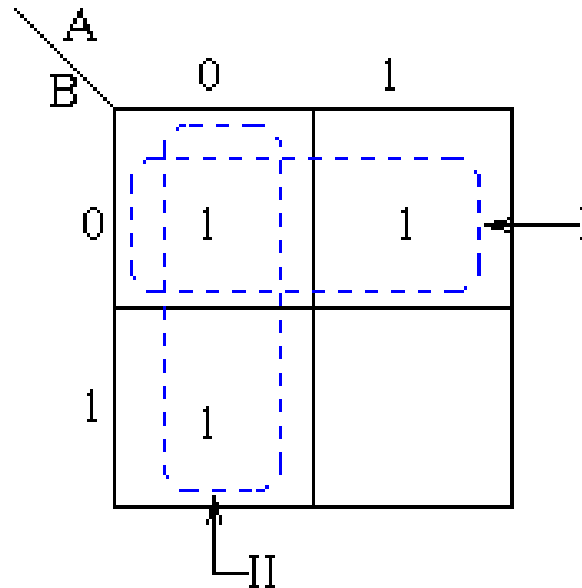
## Example 2

@ Consider the expression  $Z = \overline{A} \cdot \overline{B} + A\overline{B} + \overline{A}B$




@ Pairs of 1's are *grouped* as shown above, and the simplified answer is obtained by using the following steps:

@ Notice that a 1 can belong to more than one group
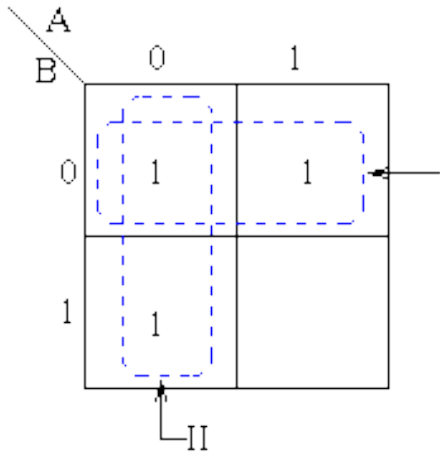
## Example 2


@  $Z = \overline{A}.\overline{B} + A\overline{B} + \overline{A}B$



- @ The first group labelled I, consists of two 1s which correspond to  $A = 0, B = 0$  and  $A = 1, B = 0$
- @ Put in another way, all squares that correspond to the area of the map where  $B = 0$  contains 1s, independent of the value of A
- @ So **when  $B = 0$  the output is 1**
- @ The expression of the **output will contain** the term  $\overline{B}$
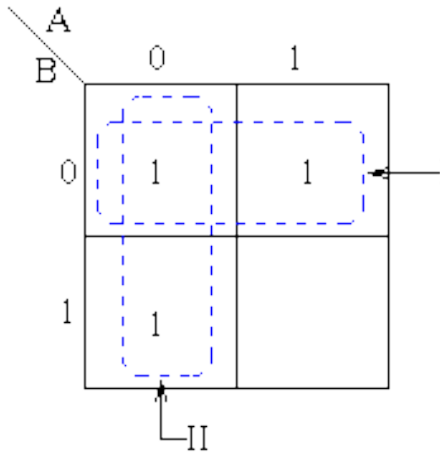
## Example 2

ⓐ  $Z = \overline{A} \cdot \overline{B} + A\overline{B} + \overline{A}B$



- ⓐ For group labelled I corresponds to the area of the map where  $A = 0$
- ⓐ The group can therefore be defined as  $\overline{A}$ 
  - This implies that when  $A = 0$  the output is 1
- ⓐ The **output is therefore 1 whenever  $B = 0$  and  $A = 0$**
- ⓐ Hence the simplified answer is  $Z = \overline{A} + \overline{B}$

# Examples with more than 2 variables

Let's start with simple...

A	B	C	Z
0	0	0	0
0	0	1	0
0	1	0	0
0	1	1	1
1	0	0	0
1	0	1	1
1	1	0	1
1	1	1	1

# Examples with more than 2 variables

Let's start with simple...


A	B	C	Z
0	0	0	0
0	0	1	0
0	1	0	0
0	1	1	1
1	0	0	0
1	0	1	1
1	1	0	1
1	1	1	1

		BC			
		00	01	11	10
A	0	0	0	1	0
	1	0	1	1	1

# Examples with more than 2 variables

Let's start with simple...


A	B	C	Z
0	0	0	0
0	0	1	0
0	1	0	0
0	1	1	1
1	0	0	0
1	0	1	1
1	1	0	1
1	1	1	1

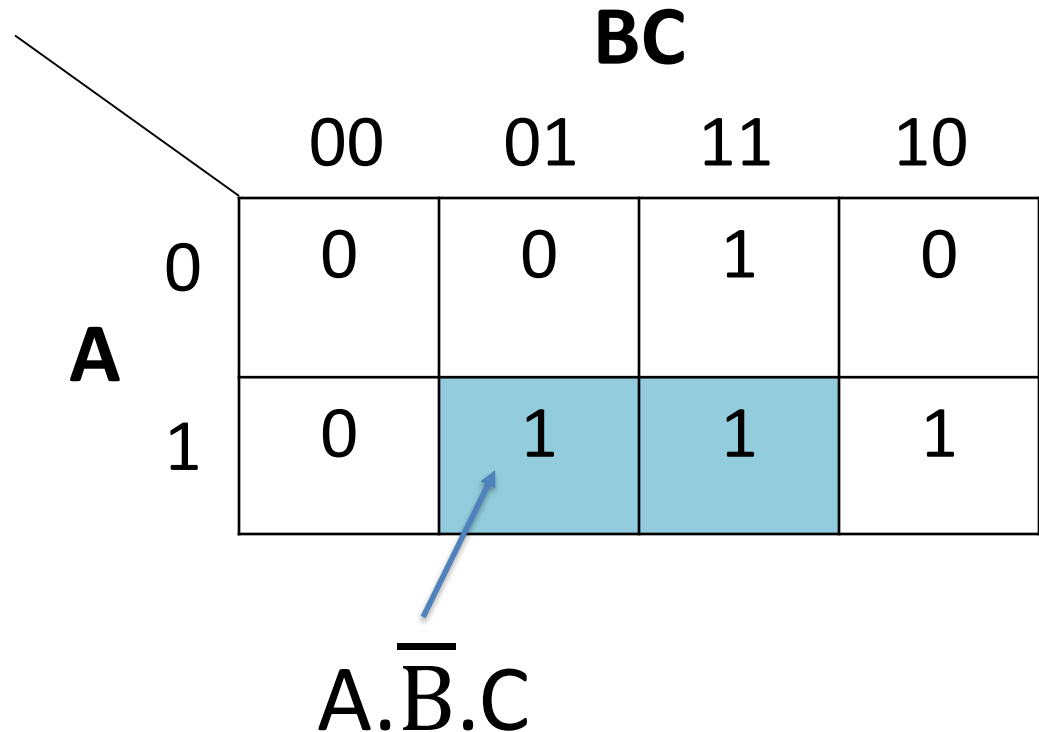

# Examples with more than 2 variables

Let's start with simple...


A	B	C	Z
0	0	0	0
0	0	1	0
0	1	0	0
0	1	1	1
1	0	0	0
1	0	1	1
1	1	0	1
1	1	1	1

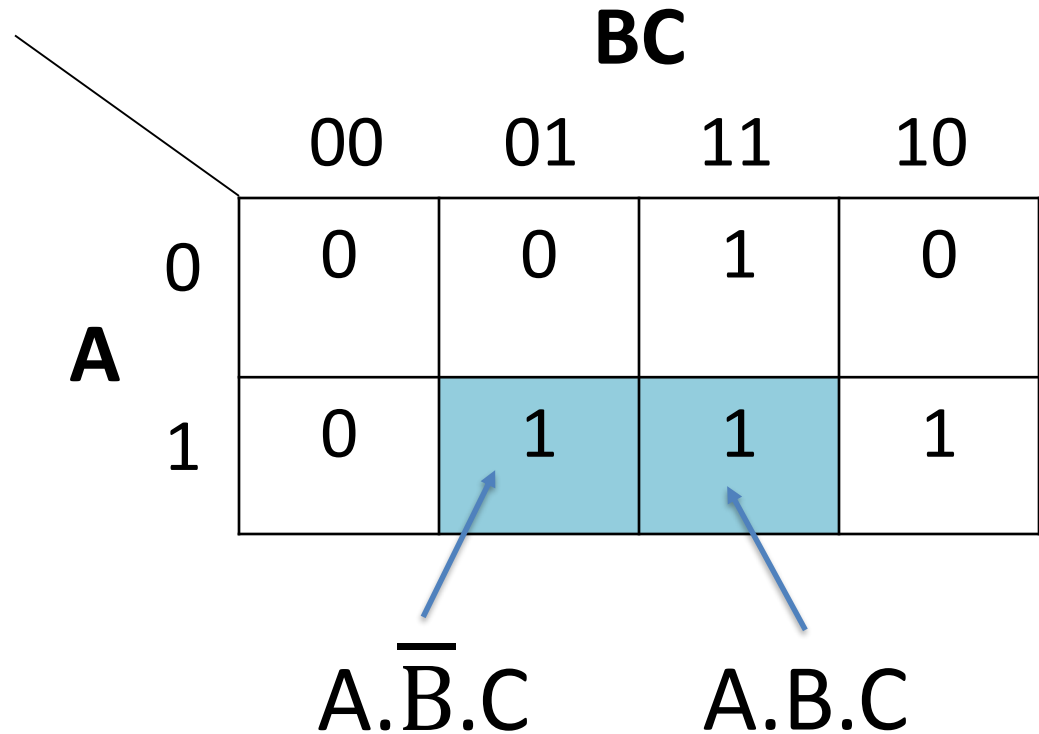

# Examples with more than 2 variables

Let's start with simple...

A	B	C	Z
0	0	0	0
0	0	1	0
0	1	0	0
0	1	1	1
1	0	0	0
1	0	1	1
1	1	0	1
1	1	1	1

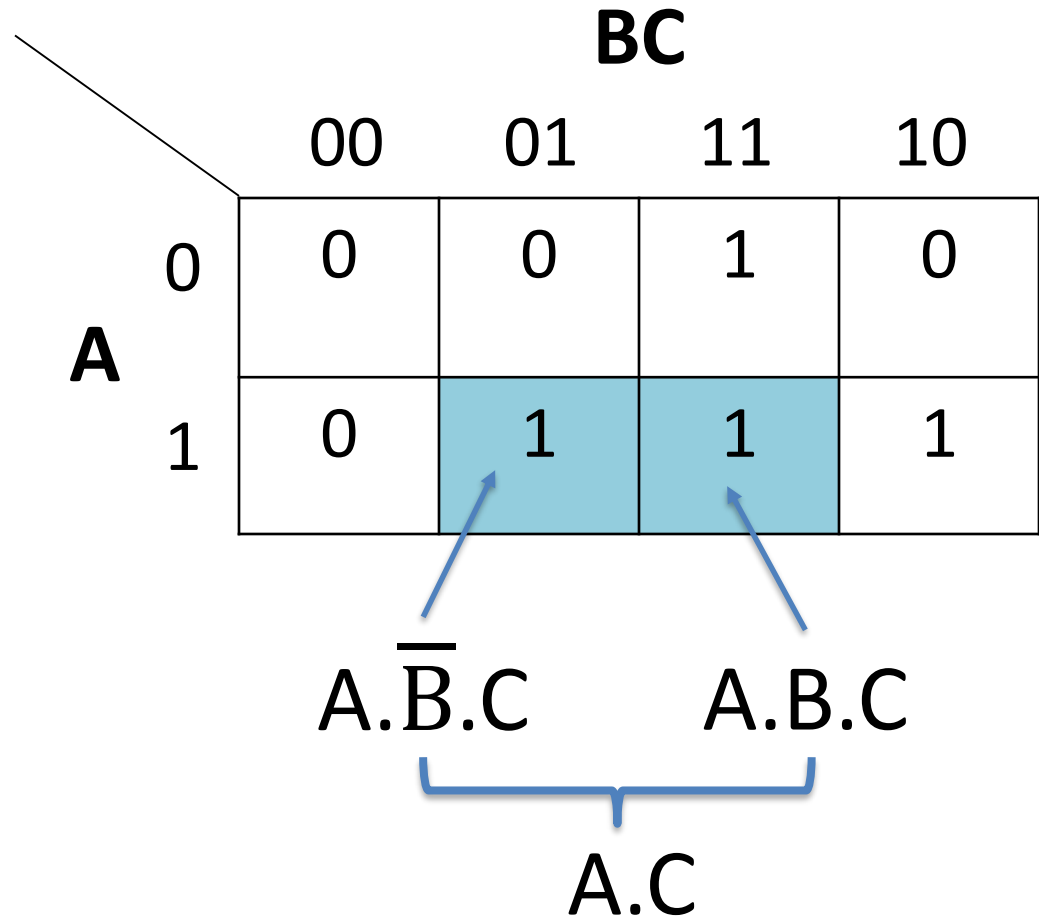



# Examples with more than 2 variables

Let's start with simple...

A	B	C	Z
0	0	0	0
0	0	1	0
0	1	0	0
0	1	1	1
1	0	0	0
1	0	1	1
1	1	0	1
1	1	1	1

		BC			
		00	01	11	10
A	0	0	0	1	0
	1	0	1	1	1

Accordingly....

A.B

# Examples with more than 2 variables

Let's start with simple...

A	B	C	Z
0	0	0	0
0	0	1	0
0	1	0	0
0	1	1	1
1	0	0	0
1	0	1	1
1	1	0	1
1	1	1	1

		BC			
		00	01	11	10
A	0	0	0	1	0
	1	0	1	1	1
		B.C			

# Examples with more than 2 variables

⊗  $Z = \overline{A} \cdot \overline{B} \cdot \overline{C} + \overline{A} \cdot B + AB\overline{C} + AC$

		AB			
		00	01	11	10
C	0	1	1	1	
	1		1	1	1

# Karnaugh Maps - Rules of Simplification

- Ⓢ The Karnaugh map uses the following rules for the simplification of expressions by grouping together adjacent cells containing ones
  - Groups may not include any cell containing a zero

A \ B	0	1
	0	1
0	0	
1	1	


WRONG ✗

A \ B	0	1
	0	1
0	0	
1	1	1

RIGHT ✓




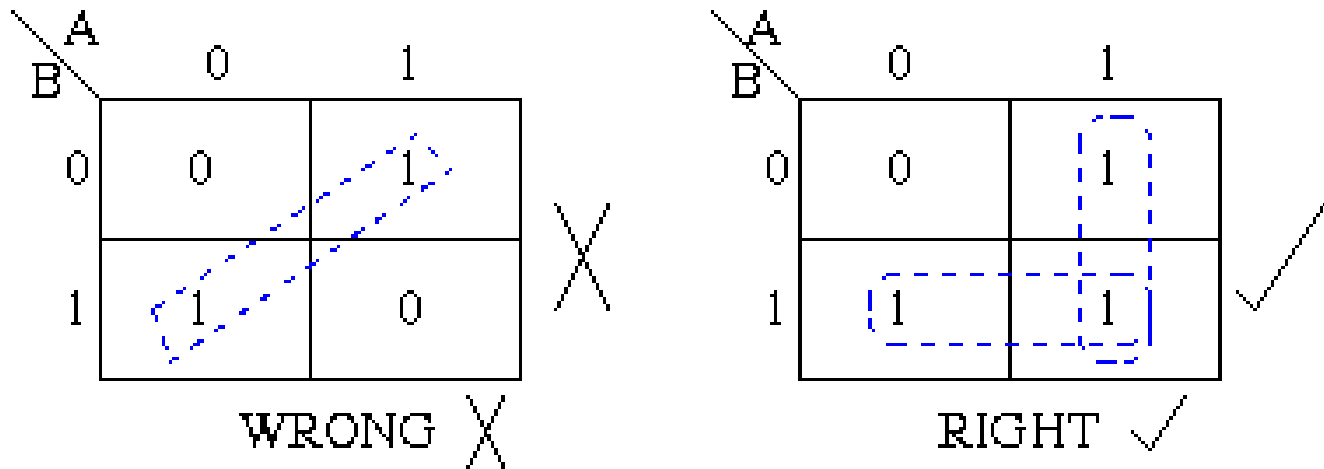
# Karnaugh Maps - Rules of Simplification

- Groups may be horizontal or vertical, but not diagonal


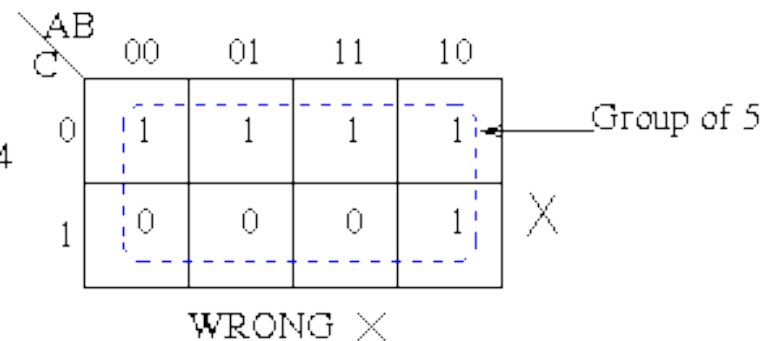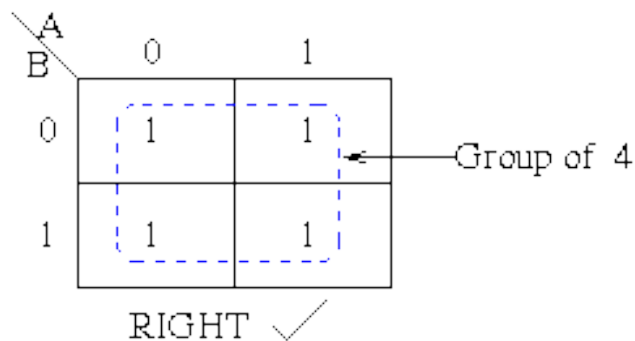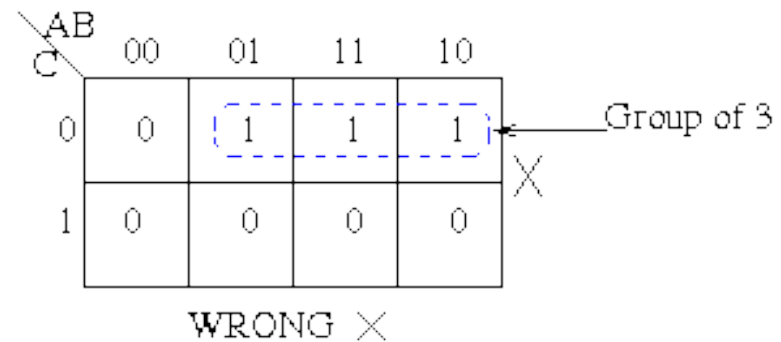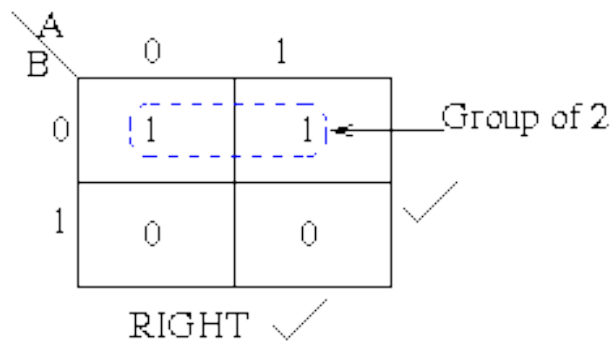
# Karnaugh Maps - Rules of Simplification


- ④ Groups must contain 1, 2, 4, 8, or in general  $2^n$  cells
  - That is if  $n = 1$ , a group will contain two 1's since  $2^1 = 2$
  - If  $n = 2$ , a group will contain four 1's since  $2^2 = 4$



# Karnaugh Maps - Rules of Simplification


- Each group should be as large as possible

		AB			
		00	01	11	10
C	0	1	1	1	1
	1	0	0	1	1

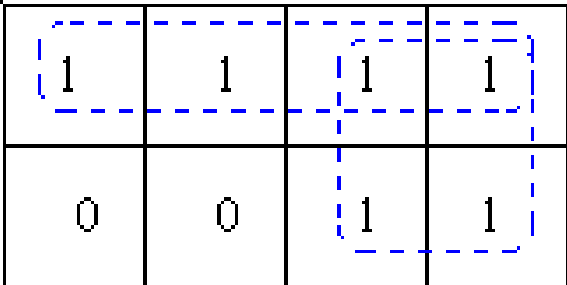

RIGHT ✓

		AB			
		00	01	11	10
C	0	1	1	1	1
	1	0	0	1	1

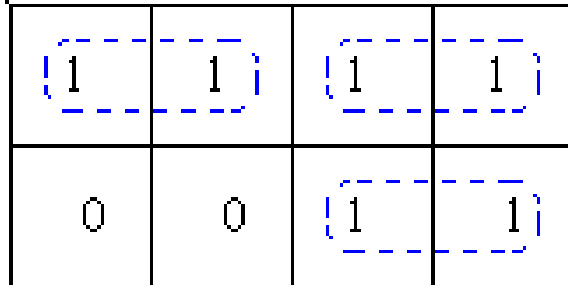


WRONG ✗

(Note that no Boolean laws broken,  
but not sufficiently minimal)
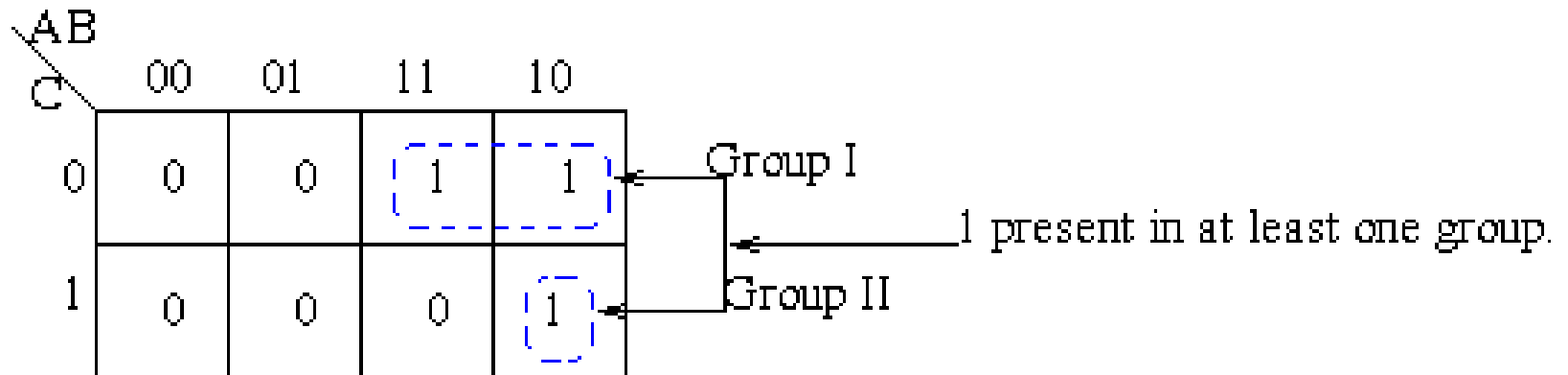
# Karnaugh Maps - Rules of Simplification



- Each cell containing a one must be in at least one group






# Karnaugh Maps - Rules of Simplification

## @ Groups may overlap

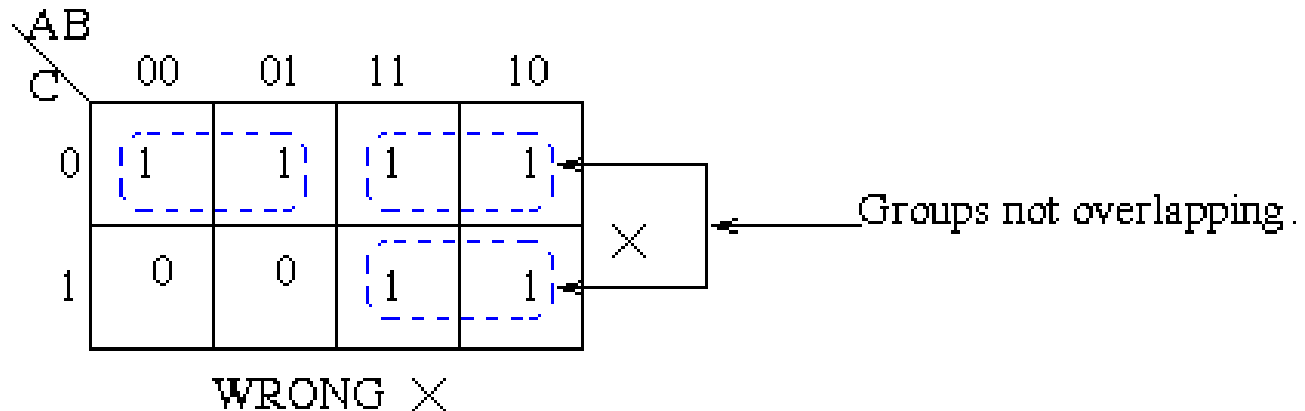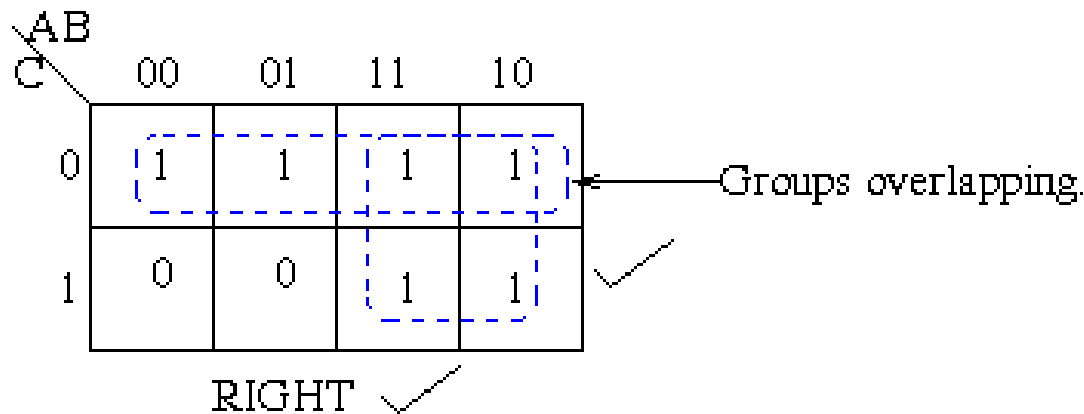
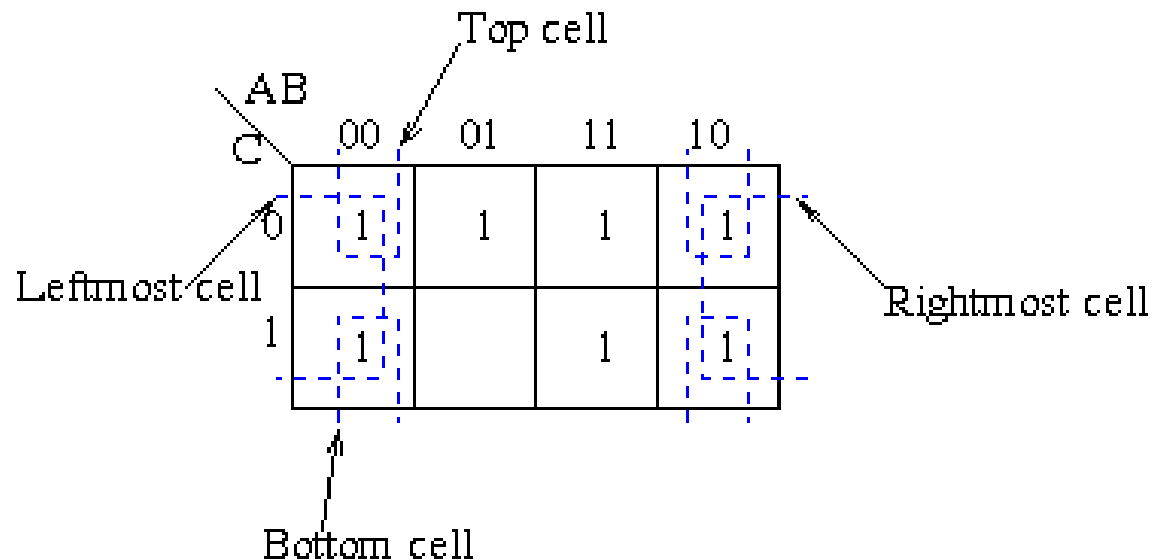
# Karnaugh Maps - Rules of Simplification

- Ⓢ Groups may wrap around the table
- Ⓢ The leftmost cell in a row may be grouped with the rightmost cell and the top cell in a column may be grouped with the bottom cell



# Karnaugh Maps - Rules of Simplification

- There should be as few groups as possible, as long as this does not contradict any of the previous rules

C \ AB	AB			
	00	01	11	10
0	1	1	1	1
1	0	0	1	1

RIGHT ✓

C \ AB	AB			
	00	01	11	10
0	1	1	1	1
1	0	0	1	1

WRONG ✗

# Summary

- @ No zeros allowed
- @ No diagonals
- @ Only power of 2 number of cells in each group
- @ Groups should be as large as possible
- @ Every one (1) must be in at least one group
- @ Overlapping allowed
- @ Wrap around allowed
- @ Fewest number of groups possible

# Examples

		BC			
		00	01	11	10
A	0	1	0	0	0
	1	1	1	0	1

$A \cdot \overline{B}$

# Examples

		BC			
		00	01	11	10
A	0	1	0	0	0
	1	1	1	0	1

$\overline{B}.\overline{C}$

# Examples

		BC			
		00	01	11	10
A	0	1	0	0	0
	1	1	1	0	1

$A.\bar{C}$

# Examples with more than 2 variables

⊗  $Z = \bar{A}.B + B.\bar{C} + B.C + A.\bar{B}.\bar{C}$

AB \ C		00	01	11	10
C	0		1	1	1
	1		1	1	



## Examples with more than 2 variables

⊙  $Z = \bar{A}.B + B.\bar{C} + B.C + A.\bar{B}.\bar{C}$

AB \ C		AB			
		00	01	11	10
C	0		1	1	1
	1		1	1	

⊙ The minimized result obtained is  $B + A\bar{C}$

# Examples with more than 2 variables

Ⓢ  $Z = \overline{A} \cdot \overline{B} \cdot \overline{C} + \overline{A} \cdot B + AB\overline{C} + AC$

AB \ C		00	01	11	10
		0	1	0	1
C	0	1	1	1	
	1		1	1	1


# Examples with more than 2 variables

⊗  $Z = \overline{A} \cdot \overline{B} \cdot \overline{C} + \overline{A} \cdot B + AB\overline{C} + AC$

AB \ C		AB			
		00	01	11	10
C	0	1	1	1	
	1		1	1	1

⊗ The minimized result obtained is  $B + AC + \overline{A} \cdot \overline{C}$

# Examples with 3 variables

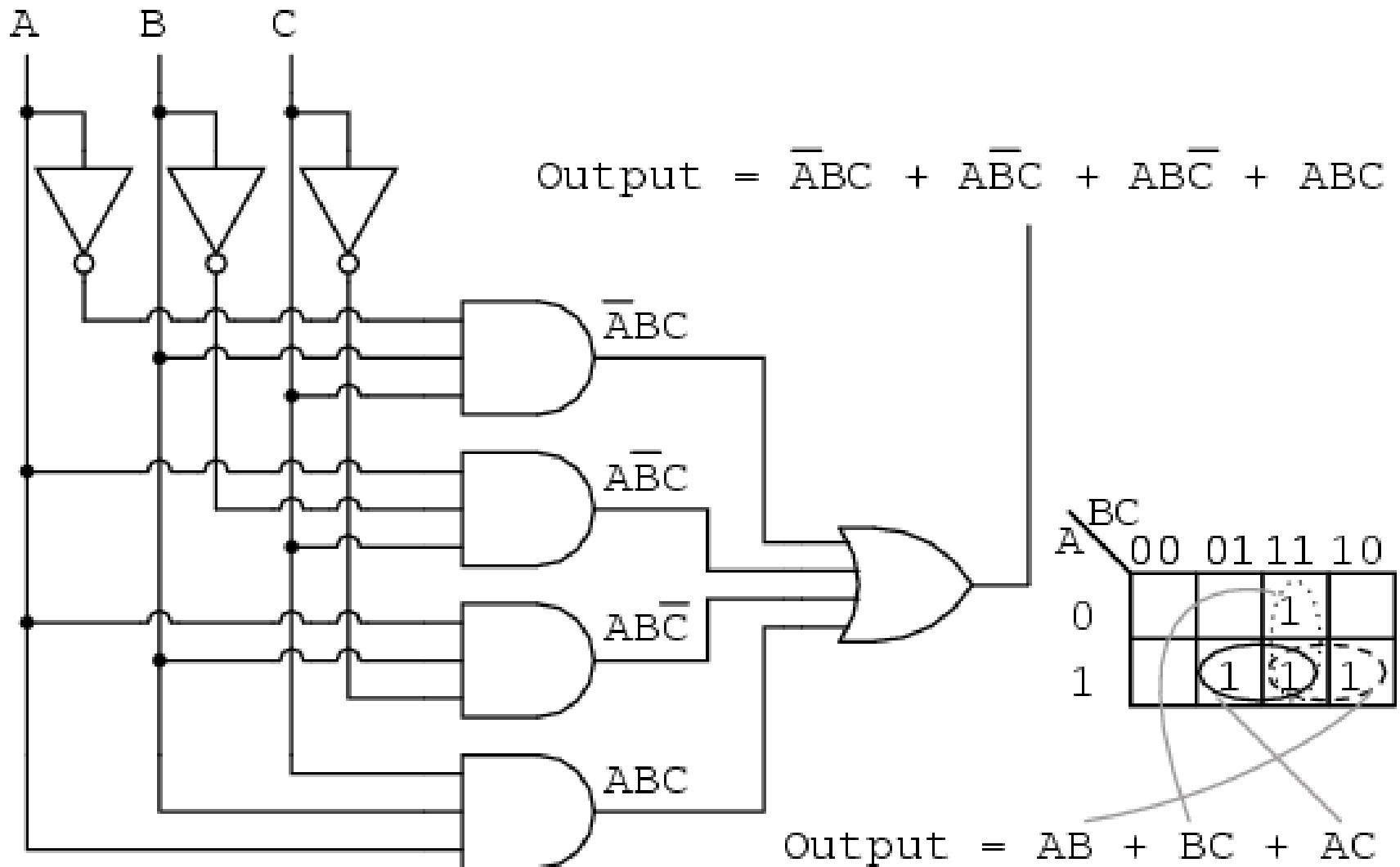

# Examples with 4 variables

		CD			
		00	01	11	10
AB	00	1	0	0	1
	01	1	1	0	0
	11	1	0	0	0
	10	1	0	0	1

# Examples with 4 variables

		CD			
		00	01	11	10
AB	00	0	0	0	0
	01	1	1	0	0
	11	0	0	0	0
	10	0	0	0	0

- ⊙ The variable D changes from a 0 to a 1 as you move from the left cell to the right cell
- ⊙ Consequently, these two 1s are not dependent upon the value of D, and therefore:
- ⊙ **D will not appear in the product term that results**
- ⊙ The Result is  **$Z = \overline{A} \cdot B \cdot \overline{C}$**

# Examples with 4 variables

		CD			
		00	01	11	10
AB	00	0	0	0	0
	01	0	0	0	0
	11	0	1	0	0
	10	0	1	0	0

@ Accordingly:

@ The Result is  $Z = A \cdot \bar{C} \cdot D$

# More Examples

		CD			
		00	01	11	10
AB	00	0	0	0	0
	01	0	0	0	0
	11	0	1	1	0
	10	0	1	1	0

@ Answer:  $Z = A.D$



# More Examples

		CD			
		00	01	11	10
AB	00	0	0	0	0
	01	0	1	1	0
	11	0	1	1	0
	10	0	0	0	0

@ Answer:  $Z = B.D$

# More Examples

		CD			
		00	01	11	10
AB	00	0	0	0	0
	01	1	1	1	1
	11	0	0	0	0
	10	0	0	0	0

© Answer:  $Z = \bar{A}.B$

# More Examples

		CD			
		00	01	11	10
AB	00	0	0	0	0
	01	1	1	1	1
	11	1	1	1	1
	10	0	0	0	0

@ Answer:  $Z = B$

# Examples with 4 variables

		CD			
		00	01	11	10
AB	00	1	0	0	1
	01	0	0	0	0
	11	0	0	0	0
	10	1	0	0	1

- ⊙ In the upper left:  $z = \overline{A} \cdot \overline{B} \cdot \overline{C} \cdot \overline{D}$ .
- ⊙ In the upper right:  $z = \overline{A} \cdot \overline{B} \cdot C \cdot \overline{D}$ .
- ⊙ In the lower left:  $z = A \cdot \overline{B} \cdot \overline{C} \cdot \overline{D}$ .
- ⊙ In the lower right:  $z = A \cdot \overline{B} \cdot C \cdot \overline{D}$ .

# Examples with 4 variables

		CD			
		00	01	11	10
AB	00	1	0	0	1
	01	0	0	0	0
	11	0	0	0	0
	10	1	0	0	1

- ⊙ In the upper left:  $z = \overline{A} \cdot \overline{B} \cdot \overline{C} \cdot \overline{D}$ .
- ⊙ In the upper right:  $z = \overline{A} \cdot \overline{B} \cdot C \cdot \overline{D}$ .
- ⊙ In the lower left:  $z = A \cdot \overline{B} \cdot \overline{C} \cdot \overline{D}$ .
- ⊙ In the lower right:  $z = A \cdot \overline{B} \cdot C \cdot \overline{D}$ .
- ⊙ By combining the first two terms above:  $z = \overline{A} \cdot \overline{B} \cdot \overline{D}$ .
- ⊙ By combining the last two terms above:  $z = A \cdot \overline{B} \cdot \overline{D}$ .
- ⊙ Then, these two terms can be combined to give:  $z = \overline{B} \cdot \overline{D}$ .

# Further Observations

		CD			
		00	01	11	10
AB	00	0	0	0	0
	01	0	1	1	1
	11	0	1	0	0
	10	0	1	0	0

@ There may well be more than one solution of equal complexity


@  $A \cdot \bar{C} \cdot D + \bar{A} \cdot B \cdot C$  ?

# Further Observations

		CD			
		00	01	11	10
AB	00	1	0	0	0
	01	0	0	1	1
	11	0	1	0	0
	10	0	1	0	0

- @ There may well be more than one solution of equal complexity
- @  $A \cdot \bar{C} \cdot D + \bar{A} \cdot B \cdot C$  ?
- @ And what about the 1 alone?

# Problem Solving with Logic Gates

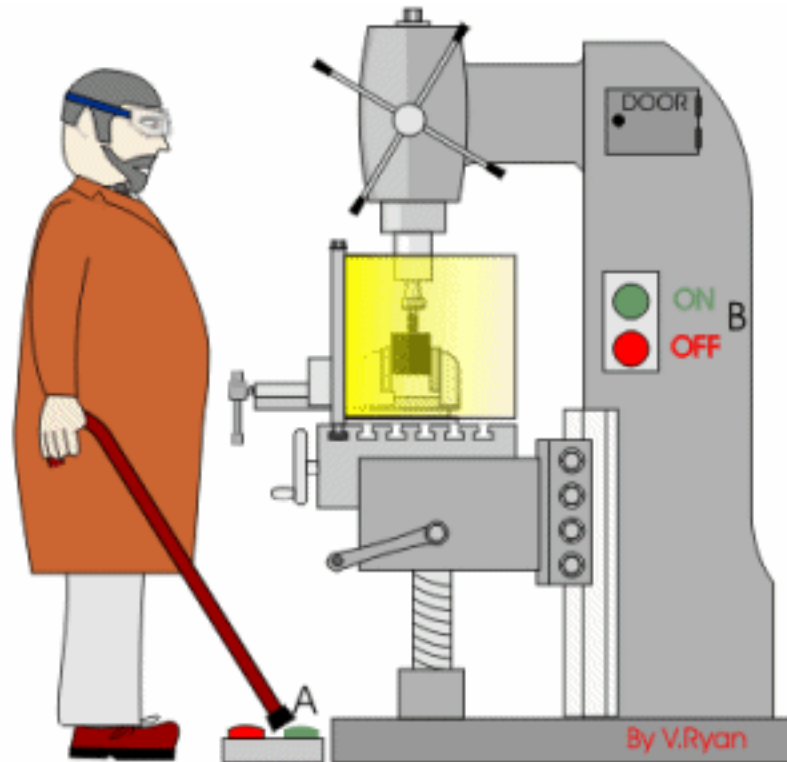




# Problem Solving with Logic Gates

- ⓐ A metal cutting milling machine has two switches, any one will allow the cutter to run.
- ⓐ The first switch is on the side of the machine and the second is a foot operated switch.
- ⓐ However, the machine has two micro-switches (used as safety devices) if any of these is released the cutter will stop.
- ⓐ The first micro-switch is on a guard, if this is opened the machine will stop.
- ⓐ The second micro-switch is on a door which allows access to the moving mechanism of the milling machine. If this is opened the machine will stop.  
The micro-switches are normally logic '1' (true, high, on) when pressed.
- ⓐ Draw the logic diagram for this machine

# Problem Solving with Logic Gates

- Ⓢ A metal cutting milling machine has two switches, any one will allow the cutter to run.
- Ⓢ The first switch is on the side of the machine and the second is a foot operated switch.
- Ⓢ However, the machine has two micro-switches (used as safety devices) if any of these is released the cutter will stop.
- Ⓢ The first micro-switch is on a guard, if this is opened the machine will stop.
- Ⓢ The second micro-switch is on a door which allows access to the moving mechanism of the milling machine. If this is opened the machine will stop. The micro-switches are normally logic '1' (true, high, on) when pressed.
- Ⓢ Draw the logic diagram for this machine


# Problem Solving with Logic Gates

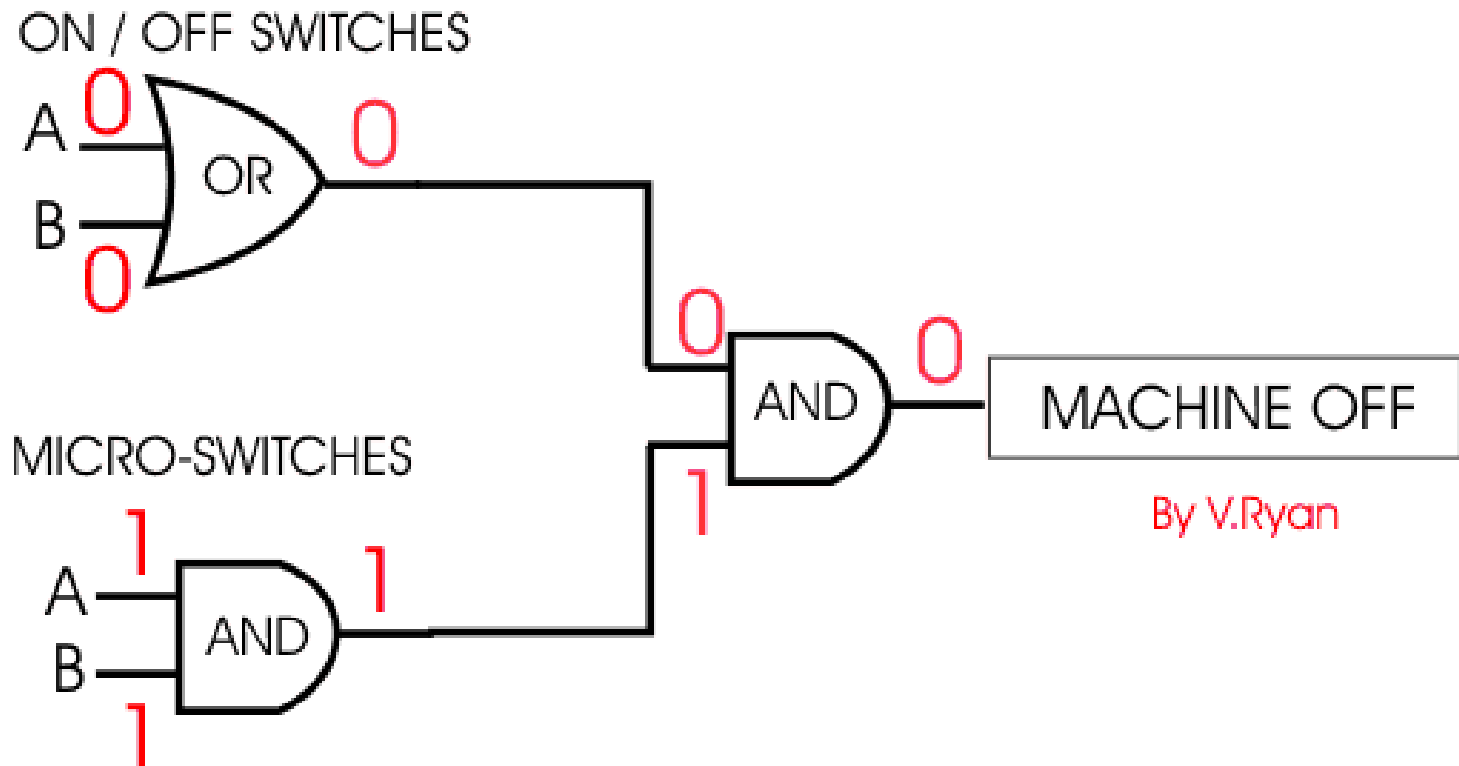

# Problem Solving with Logic Gates

- Ⓢ In addition to the above (previous) arrangement,
  - The room has two emergency stop buttons at either end of the workshop
  - If either of these are pressed all machinery in the room will stop
- Ⓢ Draw the new logic circuit for this arrangement of buttons and switches

# Problem Solving with Logic Gates

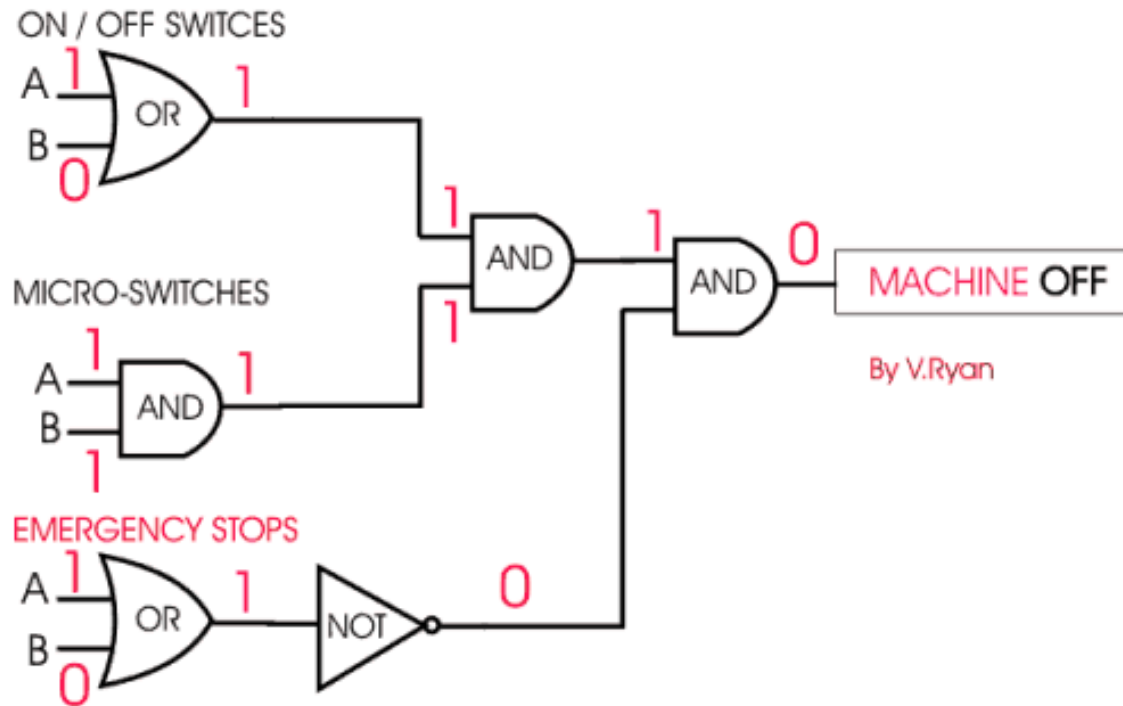

# Problem Solving with Logic Gates

- @ An engine has 4 fail-safe sensors. The engine should keep running unless any of the following condition arise:
  - If sensor 2 is activated
  - If sensor 1 and sensor 3 are activated together (meanwhile sensors 2 and 4 are inactive)
  - If sensor 3 and sensor 4 are activated together
- @ Derive the truth table for this scenario
- @ Construct a logic gate network to satisfy requirements with basic logic gates
- @ Re-design the developed logic gate network with NAND and NOR gates only

# Problem Solving with Logic Gates

- Ⓢ Conventions:
- Ⓢ A = Sensor1,  
B=Sensor2,  
C=Sensor3,  
D=Sensor4
- Ⓢ Sensor activated = 1,  
F = Shutdown=1

A	B	C	D	F
0	0	0	0	0
0	0	0	1	0
0	0	1	0	0
0	0	1	1	1
0	1	0	0	1
0	1	0	1	1
0	1	1	0	1
0	1	1	1	1
1	0	0	0	0
1	0	0	1	0
1	0	1	0	1
1	0	1	1	1
1	1	0	0	1
1	1	0	1	1
1	1	1	0	1
1	1	1	1	1

# Problem Solving with Logic Gates

		CD			
		00	01	11	10
AB	00	0	0	1	0
	01	1	1	1	1
	11	1	1	1	1
	10	0	0	1	1




# Problem Solving with Logic Gates

		CD			
		00	01	11	10
AB	00	0	0	1	0
	01	1	1	1	1
	11	1	1	1	1
	10	0	0	1	1

Ⓢ  $F = B + CD + AC$


# Problem Solving with Logic Gates

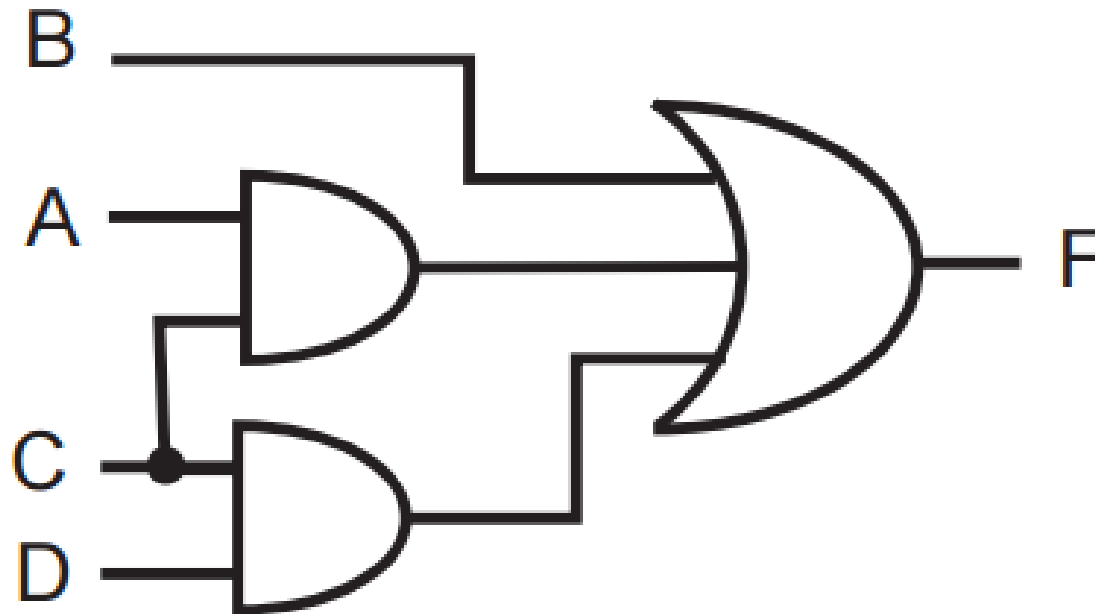
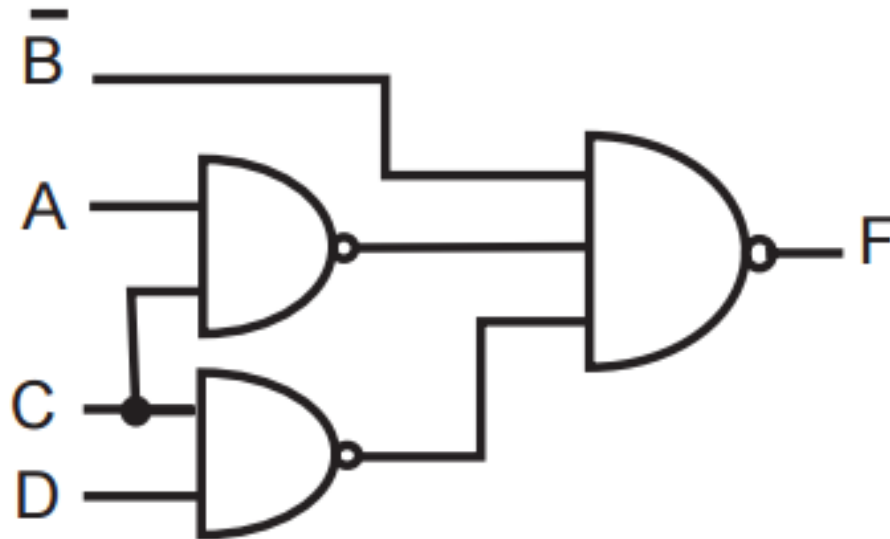
# Problem Solving with Logic Gates

Ⓢ using NAND gates only

$$F = \overline{\overline{B + CD + AC}}$$
$$= \overline{A + CD + AC} = \overline{B \cdot CD \cdot AC}$$



# Problem Solving with Logic Gates


Ⓢ using NOR gates only

$$F = B + CD + AC$$

$$F = \overline{\overline{B}} + \overline{\overline{CD}} + \overline{\overline{AC}}$$

$$F = \overline{\overline{B}} + (\overline{\overline{C} + \overline{D}}) + (\overline{\overline{A} + \overline{C}})$$
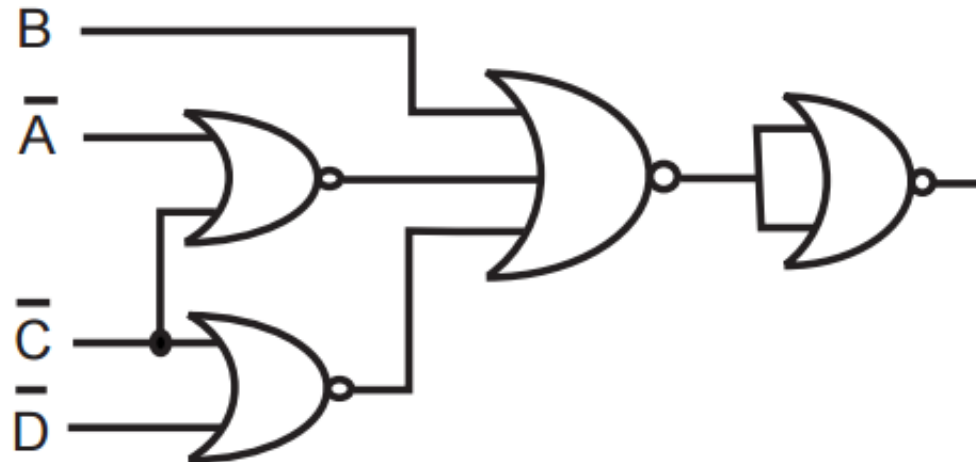
$$F = \overline{\overline{B}} = \overline{\overline{B + (\overline{\overline{C} + \overline{D}}) + (\overline{\overline{A} + \overline{C}})}}$$



# Problem Solving with Logic Gates

- Ⓢ An airbag of a vehicle is activated once the following conditions meets:
  - Engine must be running (Logic Level of sensor 'E' is High)
  - The driver / passenger has buckled-up (fasten) the seat belt (Logic level of sensor 'B' is Low)
  - Speed sensor 'S' has exceeded the threshold value. (Logic level High)
  - Vibration sensors both 'V1' and 'V2' together or 'V3' alone is triggered. (Logic level High)

# Problem Solving with Logic Gates

- Ⓢ Construct the Karnaugh Map for the scenario
- Ⓢ Construct a logic gate network to satisfy requirements with basic logic gates
- Ⓢ Re-design the developed logic gate network with NAND and NOR gates only